

Verilog Lab #4

1. 1-bit NOT gate

Design module

```
`timescale 1ns / 1ps // Specify time unit of 1 nanosecond and time precision of 1
picosecond
```

```
// 1-bit NOT gate using continuous assignment
```

```
module not_gate_cont (
    input wire a, // 1-bit input
    output wire y // 1-bit output
);
    assign y = ~a; // Continuous assignment of NOT operation
endmodule
```

```
// 1-bit NOT gate using always block
```

```
module not_gate_always (
    input wire a, // 1-bit input
    output reg y // 1-bit output (reg type for always block)
);
    always @(*) begin
        y = ~a; // Assigning NOT operation inside always block
    end
endmodule
```

Testbench module

```
`timescale 1ns / 1ps
```

```
module tb_not_gate();
    // Declare inputs for the testbench
    reg a;

    // Declare outputs for both modules
    wire y_cont;
    wire y_always;

    // Instantiate the not_gate_cont module
    not_gate_cont u1 (
```

```

        .a(a),
        .y(y_cont)
    );

    // Instantiate the not_gate_always module
    not_gate_always u2 (
        .a(a),
        .y(y_always)
    );

    // Testbench initial block
    initial begin
        // Enable VCD dumping for waveform generation
        $dumpfile("dump.vcd"); // VCD file name
        $dumpvars(0, tb_not_gate); // Dump all variables in tb_not_gate

        // Display results in the console
        $monitor("Time=%0t | a=%b | y_cont=%b | y_always=%b", $time, a, y_cont,
y_always);

        // Test case 1: a = 0
        a = 1'b0;
        #10;

        // Test case 2: a = 1
        a = 1'b1;
        #10;

        // Finish simulation
        $finish;
    end
endmodule


```

Results

```

[2024-10-22 02:44:57 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
Time=0 | a=0 | y_cont=1 | y_always=1
Time=10000 | a=1 | y_cont=0 | y_always=0
testbench.sv:41: $finish called at 20000 (1ps)
Done

```

 

Note: To revert to EPWave opening in a new browser window, set that option on your profile page.

2. 2-bits AND gate

Design module

```
`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps
```

```
// 2-bit AND gate using continuous assignment
```

```
module and_gate_cont (
    input wire [1:0] a, // 2-bit input
    input wire [1:0] b, // 2-bit input
    output wire [1:0] y // 2-bit output
);
    assign y = a & b; // Continuous assignment for AND operation
endmodule
```

```
// 2-bit AND gate using always block
```

```
module and_gate_always (
    input wire [1:0] a, // 2-bit input
    input wire [1:0] b, // 2-bit input
    output reg [1:0] y // 2-bit output (reg type for always block)
);
    always @(*) begin
        y = a & b; // AND operation inside always block
    end
endmodule
```

Testbench module

```
`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps
```

```
module tb_and_gate();
    // Declare inputs for the testbench
    reg [1:0] a;
```

```

reg [1:0] b;

// Declare outputs for both modules
wire [1:0] y_cont;
wire [1:0] y_always;

// Instantiate the and_gate_cont module
and_gate_cont u1 (
    .a(a),
    .b(b),
    .y(y_cont)
);

// Instantiate the and_gate_always module
and_gate_always u2 (
    .a(a),
    .b(b),
    .y(y_always)
);

// Testbench initial block
initial begin
    // Enable VCD dumping for waveform generation
    $dumpfile("dump.vcd");
    $dumpvars(0, tb_and_gate);

    // Display results in the console
    $monitor("Time=%0t | a=%b | b=%b | y_cont=%b | y_always=%b", $time, a, b,
y_cont, y_always);

    // Test case 1: a = 00, b = 00
    a = 2'b00; b = 2'b00;
    #10;

    // Test case 2: a = 01, b = 10
    a = 2'b01; b = 2'b10;
    #10;

    // Test case 3: a = 11, b = 11
    a = 2'b11; b = 2'b11;

```

```

#10;

// Test case 4: a = 10, b = 01
a = 2'b10; b = 2'b01;
#10;

// Finish simulation
$finish;
end
endmodule


```

Results

```

[2024-10-22 02:53:33 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
Time=0 | a=00 | b=00 | y_cont=00 | y_always=00
Time=10000 | a=01 | b=10 | y_cont=00 | y_always=00
Time=20000 | a=11 | b=11 | y_cont=11 | y_always=11
Time=30000 | a=10 | b=01 | y_cont=00 | y_always=00
testbench.sv:52: $finish called at 40000 (1ps)
Done

```

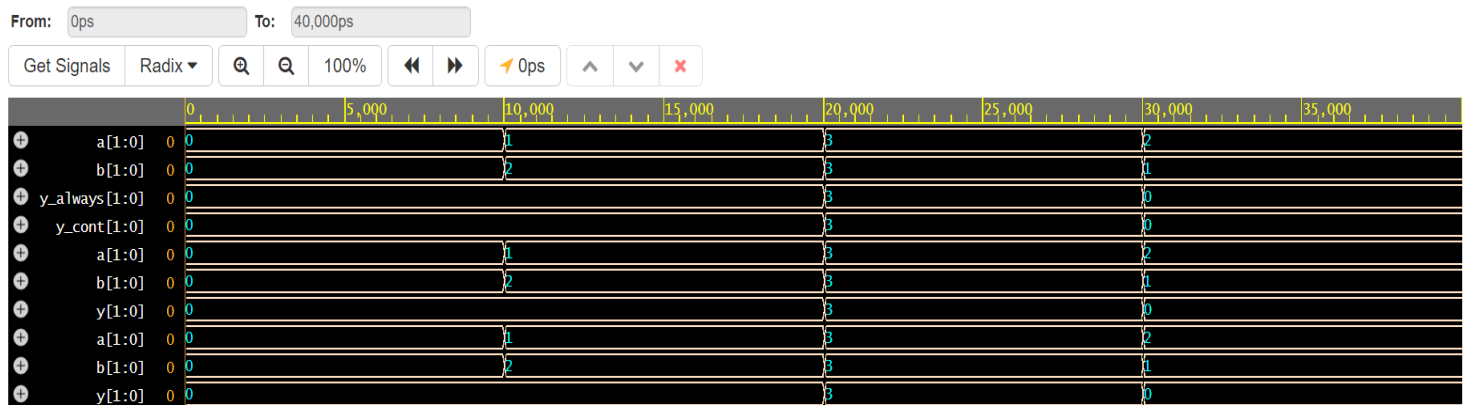

Note: To revert to EPWave opening in a new browser window, set that option on your profile page.

3. 2-bits OR gate

Design module

```
`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps
```

```

module tb_or_gate();
    // Declare inputs for the testbench
    reg [1:0] a;
    reg [1:0] b;

    // Declare outputs for both modules

```

```

wire [1:0] y_cont;
wire [1:0] y_always;

// Instantiate the or_gate_cont module
or_gate_cont u1 (
    .a(a),
    .b(b),
    .y(y_cont)
);

// Instantiate the or_gate_always module
or_gate_always u2 (
    .a(a),
    .b(b),
    .y(y_always)
);

// Testbench initial block
initial begin
    // Enable VCD dumping for waveform generation
    $dumpfile("dump.vcd");
    $dumpvars(0, tb_or_gate);

    // Display results in the console
    $monitor("Time=%0t | a=%b | b=%b | y_cont=%b | y_always=%b", $time, a, b,
y_cont, y_always);

    // Test case 1: a = 00, b = 00
    a = 2'b00; b = 2'b00;
    #10;

    // Test case 2: a = 01, b = 10
    a = 2'b01; b = 2'b10;
    #10;

    // Test case 3: a = 11, b = 11
    a = 2'b11; b = 2'b11;
    #10;

    // Test case 4: a = 10, b = 01

```

```

    a = 2'b10; b = 2'b01;
    #10;

    // Finish simulation
    $finish;
end
endmodule

```

Testbench module

```

`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps

```

```

module tb_or_gate();
    // Declare inputs for the testbench
    reg [1:0] a;
    reg [1:0] b;

    // Declare outputs for both modules
    wire [1:0] y_cont;
    wire [1:0] y_always;

    // Instantiate the or_gate_cont module
    or_gate_cont u1 (
        .a(a),
        .b(b),
        .y(y_cont)
    );

    // Instantiate the or_gate_always module
    or_gate_always u2 (
        .a(a),
        .b(b),
        .y(y_always)
    );

    // Testbench initial block
    initial begin
        // Enable VCD dumping for waveform generation
        $dumpfile("dump.vcd");
        $dumpvars(0, tb_or_gate);
    end
endmodule

```

```

// Display results in the console
$monitor("Time=%0t | a=%b | b=%b | y_cont=%b | y_always=%b", $time, a, b,
y_cont, y_always);

// Test case 1: a = 00, b = 00
a = 2'b00; b = 2'b00;
#10;

// Test case 2: a = 01, b = 10
a = 2'b01; b = 2'b10;
#10;

// Test case 3: a = 11, b = 11
a = 2'b11; b = 2'b11;
#10;

// Test case 4: a = 10, b = 01
a = 2'b10; b = 2'b01;
#10;

// Finish simulation
$finish;
end
endmodule

```

Results

```
[2024-10-22 03:09:38 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out
```

VCD info: dumpfile dump.vcd opened for output.

Time=0 | a=00 | b=00 | y_cont=00 | y_always=00


Time=10000 | a=01 | b=10 | y_cont=11 | y_always=11

Time=20000 | a=11 | b=11 | y_cont=11 | y_always=11

Time=30000 | a=10 | b=01 | y_cont=11 | y_always=11

testbench.sv:52: \$finish called at 40000 (1ps)

Done

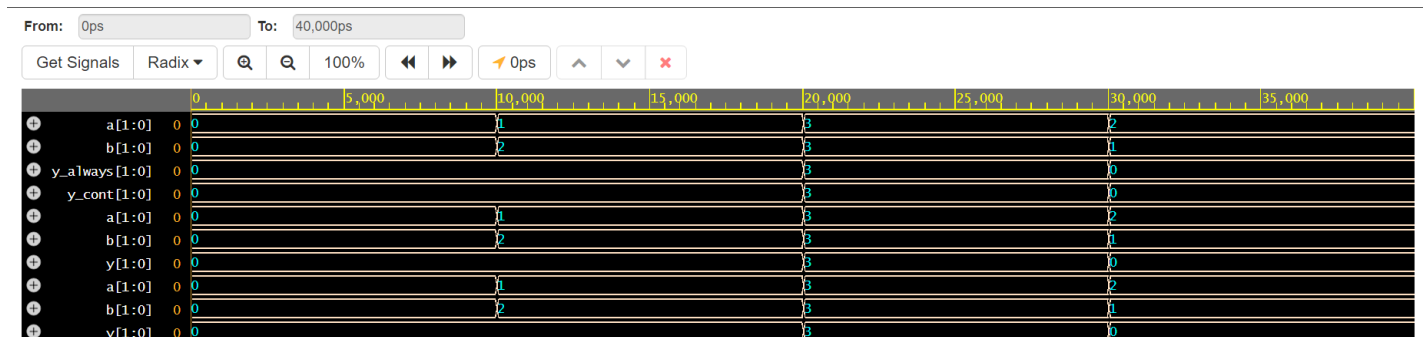

Note: To revert to EPWave opening in a new browser window, set that option on your profile page.

4. 2-bits NAND gate

Design module

```
`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps

// 2-bit NAND gate using continuous assignment
module nand_gate_cont (
    input wire [1:0] a, // 2-bit input
    input wire [1:0] b, // 2-bit input
    output wire [1:0] y // 2-bit output
);
    assign y = ~(a & b); // Continuous assignment for NAND operation
endmodule

`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps

// 2-bit NAND gate using always block
module nand_gate_always (
    input wire [1:0] a, // 2-bit input
    input wire [1:0] b, // 2-bit input
    output reg [1:0] y // 2-bit output (reg type for always block)
);
    always @(*) begin
        y = ~(a & b); // NAND operation inside always block
    end
endmodule
```

Testbench module

```
`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps

module tb_nand_gate();
    // Declare inputs for the testbench
    reg [1:0] a;
    reg [1:0] b;

    // Declare outputs for both modules
    wire [1:0] y_cont;
    wire [1:0] y_always;

    // Instantiate the nand_gate_cont module
    nand_gate_cont u1 (
```

```

        .a(a),
        .b(b),
        .y(y_cont)
    );

// Instantiate the nand_gate_always module
nand_gate_always u2 (
    .a(a),
    .b(b),
    .y(y_always)
);

// Testbench initial block
initial begin
    // Enable VCD dumping for waveform generation
    $dumpfile("dump.vcd");
    $dumpvars(0, tb_nand_gate);

    // Display results in the console
    $monitor("Time=%0t | a=%b | b=%b | y_cont=%b | y_always=%b", $time, a, b, y_cont,
y_always);

    // Test case 1: a = 00, b = 00
    a = 2'b00; b = 2'b00;
    #10;

    // Test case 2: a = 01, b = 10
    a = 2'b01; b = 2'b10;
    #10;

    // Test case 3: a = 11, b = 11
    a = 2'b11; b = 2'b11;
    #10;

    // Test case 4: a = 10, b = 01
    a = 2'b10; b = 2'b01;
    #10;

    // Finish simulation
    $finish;

```


```
end  
endmodule
```

Results

```
[2024-10-22 03:18:51 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&  
unbuffer vvp a.out
```

```
VCD info: dumpfile dump.vcd opened for output.  
Time=0 | a=00 | b=00 | y_cont=11 | y_always=11  
Time=10000 | a=01 | b=10 | y_cont=11 | y_always=11  
Time=20000 | a=11 | b=11 | y_cont=00 | y_always=00  
Time=30000 | a=10 | b=01 | y_cont=11 | y_always=11  
testbench.sv:52: $finish called at 40000 (1ps)
```

Done

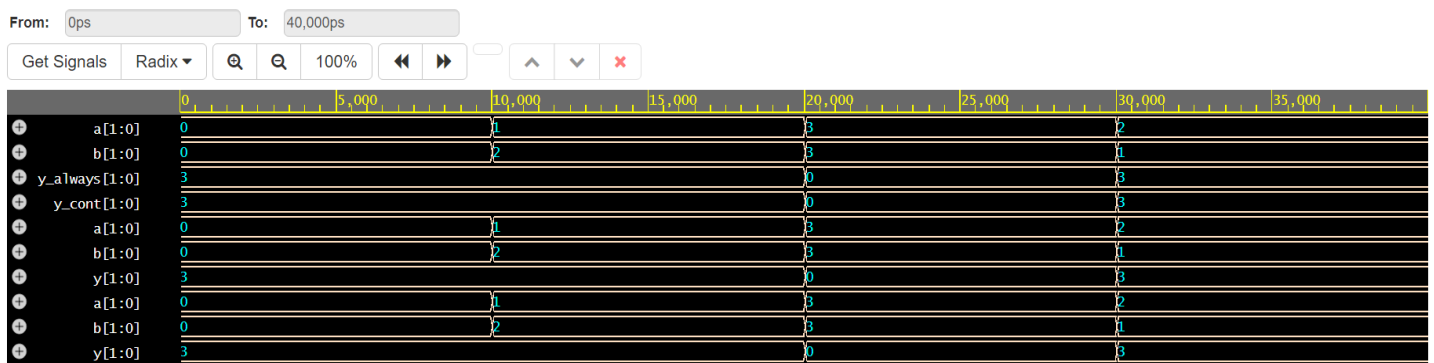

Note: To revert to EPWave opening in a new browser window, set that option on your profile page.

5. 2-bits NOR gate

Design module

```
`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps
```

```
module tb_nor_gate();  
    // Declare inputs for the testbench  
    reg [1:0] a;  
    reg [1:0] b;  
  
    // Declare outputs for both modules  
    wire [1:0] y_cont;  
    wire [1:0] y_always;  
  
    // Instantiate the nor_gate_cont module  
    nor_gate_cont u1 (  
        .a(a),  
        .b(b),  
        .y(y_cont)  
    );  
endmodule
```

```

// Instantiate the nor_gate_always module
nor_gate_always u2 (
    .a(a),
    .b(b),
    .y(y_always)
);

// Testbench initial block
initial begin
    // Enable VCD dumping for waveform generation
    $dumpfile("dump.vcd");
    $dumpvars(0, tb_nor_gate);

    // Display results in the console
    $monitor("Time=%0t | a=%b | b=%b | y_cont=%b | y_always=%b", $time, a, b,
y_cont, y_always);

    // Test case 1: a = 00, b = 00
    a = 2'b00; b = 2'b00;
    #10;

    // Test case 2: a = 01, b = 10
    a = 2'b01; b = 2'b10;
    #10;

    // Test case 3: a = 11, b = 11
    a = 2'b11; b = 2'b11;
    #10;

    // Test case 4: a = 10, b = 01
    a = 2'b10; b = 2'b01;
    #10;

    // Finish simulation
    $finish;
end
endmodule

```

Testbench module

```

`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps

module tb_nor_gate();
    // Declare inputs for the testbench
    reg [1:0] a;
    reg [1:0] b;

    // Declare outputs for both modules
    wire [1:0] y_cont;
    wire [1:0] y_always;

    // Instantiate the nor_gate_cont module
    nor_gate_cont u1 (
        .a(a),
        .b(b),
        .y(y_cont)
    );

    // Instantiate the nor_gate_always module
    nor_gate_always u2 (
        .a(a),
        .b(b),
        .y(y_always)
    );

    // Testbench initial block
    initial begin
        // Enable VCD dumping for waveform generation
        $dumpfile("dump.vcd");
        $dumpvars(0, tb_nor_gate);

        // Display results in the console
        $monitor("Time=%0t | a=%b | b=%b | y_cont=%b | y_always=%b", $time, a, b,
y_cont, y_always);

        // Test case 1: a = 00, b = 00
        a = 2'b00; b = 2'b00;
        #10;

        // Test case 2: a = 01, b = 10

```

```

a = 2'b01; b = 2'b10;
#10;

// Test case 3: a = 11, b = 11
a = 2'b11; b = 2'b11;
#10;

// Test case 4: a = 10, b = 01
a = 2'b10; b = 2'b01;
#10;

// Finish simulation
$finish;
end
endmodule

```

Results

```

[2024-10-22 03:25:56 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out

```

VCD info: dumpfile dump.vcd opened for output.

Time=0 | a=00 | b=00 | y_cont=11 | y_always=11


Time=10000 | a=01 | b=10 | y_cont=00 | y_always=00

Time=20000 | a=11 | b=11 | y_cont=00 | y_always=00

Time=30000 | a=10 | b=01 | y_cont=00 | y_always=00

testbench.sv:52: \$finish called at 40000 (1ps)

Done

 

Note: To revert to EPWave opening in a new browser window, set that option on your profile page.

6. 2-bits XOR gate

Design module

```
`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps
```

```
// 2-bit XOR gate using continuous assignment
```

```

module xor_gate_cont (
    input wire [1:0] a, // 2-bit input
    input wire [1:0] b, // 2-bit input
    output wire [1:0] y // 2-bit output
);
    assign y = a ^ b; // Continuous assignment for XOR operation
endmodule

```

```

`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps

```

```

// 2-bit XOR gate using always block

```

```

module xor_gate_always (
    input wire [1:0] a, // 2-bit input
    input wire [1:0] b, // 2-bit input
    output reg [1:0] y // 2-bit output (reg type for always block)
);
    always @(*) begin
        y = a ^ b; // XOR operation inside always block
    end
endmodule

```

Testbench module

```

`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps

```

```

module tb_xor_gate();
    // Declare inputs for the testbench
    reg [1:0] a;
    reg [1:0] b;

    // Declare outputs for both modules
    wire [1:0] y_cont;
    wire [1:0] y_always;

    // Instantiate the xor_gate_cont module
    xor_gate_cont u1 (
        .a(a),
        .b(b),
        .y(y_cont)
    );

```

```

// Instantiate the xor_gate_always module
xor_gate_always u2 (
    .a(a),
    .b(b),
    .y(y_always)
);

// Testbench initial block
initial begin
    // Enable VCD dumping for waveform generation
    $dumpfile("dump.vcd");
    $dumpvars(0, tb_xor_gate);

    // Display results in the console
    $monitor("Time=%0t | a=%b | b=%b | y_cont=%b | y_always=%b", $time, a, b,
y_cont, y_always);

    // Test case 1: a = 00, b = 00
    a = 2'b00; b = 2'b00;
    #10;

    // Test case 2: a = 01, b = 10
    a = 2'b01; b = 2'b10;
    #10;

    // Test case 3: a = 11, b = 11
    a = 2'b11; b = 2'b11;
    #10;

    // Test case 4: a = 10, b = 01
    a = 2'b10; b = 2'b01;
    #10;

    // Finish simulation
    $finish;
end
endmodule

```

Results


```

[2024-10-22 03:31:23 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out

```



```
VCD info: dumpfile dump.vcd opened for output.
Time=0 | a=00 | b=00 | y_cont=00 | y_always=00
Time=10000 | a=01 | b=10 | y_cont=11 | y_always=11
Time=20000 | a=11 | b=11 | y_cont=00 | y_always=00
Time=30000 | a=10 | b=01 | y_cont=11 | y_always=11
testbench.sv:52: $finish called at 40000 (1ps)
Done
```

 

Note: To revert to EPWave opening in a new browser window, set that option on your profile page.

7. 2-bits XNOR gate

Design module

```
`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps
```

```
// 2-bit XNOR gate using continuous assignment
```

```
module xnor_gate_cont (
    input wire [1:0] a, // 2-bit input
    input wire [1:0] b, // 2-bit input
    output wire [1:0] y // 2-bit output
);
    assign y = ~(a ^ b); // Continuous assignment for XNOR operation
endmodule
```

```
`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps
```

```
// 2-bit XNOR gate using always block
```

```
module xnor_gate_always (
    input wire [1:0] a, // 2-bit input
    input wire [1:0] b, // 2-bit input
    output reg [1:0] y // 2-bit output (reg type for always block)
);
    always @(*) begin
```

```

        y = ~(a ^ b);    // XNOR operation inside always block
    end
endmodule

```

Testbench module

```

`timescale 1ns / 1ps // Time unit is 1ns, and time precision is 1ps

```

```

module tb_xnor_gate();
    // Declare inputs for the testbench
    reg [1:0] a;
    reg [1:0] b;

    // Declare outputs for both modules
    wire [1:0] y_cont;
    wire [1:0] y_always;

    // Instantiate the xnor_gate_cont module
    xnor_gate_cont u1 (
        .a(a),
        .b(b),
        .y(y_cont)
    );

    // Instantiate the xnor_gate_always module
    xnor_gate_always u2 (
        .a(a),
        .b(b),
        .y(y_always)
    );

    // Testbench initial block
    initial begin
        // Enable VCD dumping for waveform generation
        $dumpfile("dump.vcd");
        $dumpvars(0, tb_xnor_gate);

        // Display results in the console
        $monitor("Time=%0t | a=%b | b=%b | y_cont=%b | y_always=%b", $time, a, b,
            y_cont, y_always);
    end
endmodule

```

```

// Test case 1: a = 00, b = 00
a = 2'b00; b = 2'b00;
#10;

// Test case 2: a = 01, b = 10
a = 2'b01; b = 2'b10;
#10;

// Test case 3: a = 11, b = 11
a = 2'b11; b = 2'b11;
#10;

// Test case 4: a = 10, b = 01
a = 2'b10; b = 2'b01;
#10;

// Finish simulation
$finish;
end
endmodule

```

Results

```

[2024-10-22 03:36:02 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv &&
unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
Time=0 | a=00 | b=00 | y_cont=11 | y_always=11
Time=10000 | a=01 | b=10 | y_cont=00 | y_always=00
Time=20000 | a=11 | b=11 | y_cont=11 | y_always=11
Time=30000 | a=10 | b=01 | y_cont=00 | y_always=00
testbench.sv:52: $finish called at 40000 (1ps)
Done

```

From: 0ps To: 40,000ps

Get Signals


Radix ▾

🔍 🔍 100%

⏮ ⏭

⏪ ⏩

⏮ ⏭

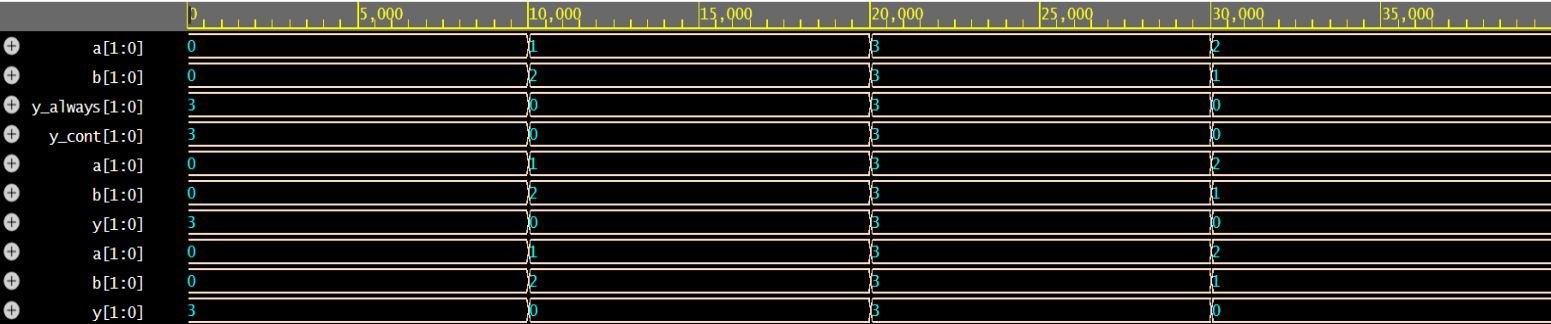

Note: To revert to EPWave opening in a new browser window, set that option on your profile page.